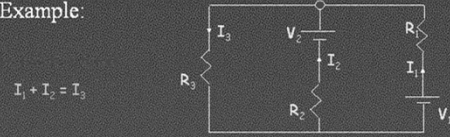


Kirchhoff's Rules

- Kirchhoff's Junction Rule:
 -
- Kirchhoff's Loop Rule:
 -


The Junction Rule

- Conceptual Basis: conservation of charge
- At any junction in a circuit, the current that enters the junction equals the current that leaves the junction.
- Example:



The Loop Rule

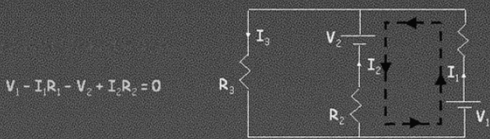- Conceptual Basis: conservation of energy
- Going around any complete loop in a circuit, the sum total of all the potential differences is zero.
- Example:



Using Kirchhoff's Rules

- (1) Label all currents
- (2) Write down junction equation $I_{in} = I_{out}$


- (3) Choose loop and direction

- Choose any direction
- You will need one less loop than unknown currents

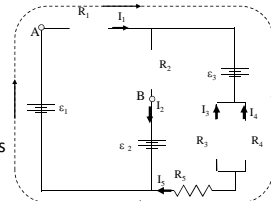- (4) Write down voltage changes

Be careful about signs


- For batteries – voltage change is positive when summing from negative to positive
- For resistors – voltage change is negative when summing in the direction of the current



Example



Loop Rule Practice

Find I:

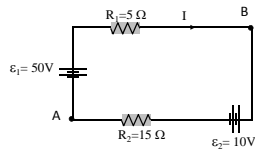

Resistors R1 and R2 are

1. In parallel
2. In series
3. neither

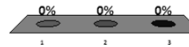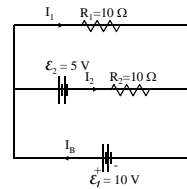

How would I_1 change if the switch was opened?

1. Increase
2. No change
3. Decrease

$\mathcal{E}_1 = 10 \text{ V}$

$\mathcal{E}_2 = 5 \text{ V}$

$R = 10 \Omega$

$R = 10 \Omega$

$R = 10 \Omega$

I_1

I_2

I_3

0% 0% 0%

1 2 3

Checkpoint

How do I know the direction of I_2 ?

It doesn't matter. Choose whatever direction you like. Then solve the equations to find I_2 . If the result is positive, then your initial guess was correct. If result is negative, then actual direction is opposite to your initial guess.

Work through checkpoint with opposite sign for I_2 ?

$+\mathcal{E}_1 - \mathcal{E}_2 + I_2 R = 0$ Note the sign change from last slide

$\Rightarrow I_2 = -0.5 \text{ A}$ Answer has same magnitude as before but opposite sign. That means current goes to the left, as we found before.

Kirchhoff's Junction Rule

Current Entering = Current Leaving

$I_1 = I_2 + I_3$

Checkpoint

1) $I_B = 0.5 \text{ A}$ 2) $I_B = 1.0 \text{ A}$ 3) $I_B = 1.5 \text{ A}$

$I_B = I_1 + I_2 = 1.5 \text{ A}$

"The first two can be calculated using $V=IR$ because the voltage and resistance is given, and the current through E_1 can be calculated with the help of Kirchhoff's Junction rule, that states whatever current flows into the junction must flow out. So I_1 and I_2 are added together."

Kirchhoff's Laws

- (1) Label all currents
Choose any direction
- (2) Write down the junction equation
 $I_{in} = I_{out}$
- (3) Choose loop and direction
Your choice!
- (4) Write down voltage changes
Follow any loops
- (5) Solve the equations by substitution or combination.

Example

You try it!

In the circuit below you are given \mathcal{E}_1 , \mathcal{E}_2 , R_1 , R_2 and R_3 . Find I_1 , I_2 and I_3 .

Example

Let's put in actual numbers

In the circuit below you are given \mathcal{E}_1 , \mathcal{E}_2 , R_1 , R_2 and R_3 . Find I_1 , I_2 and I_3 .

1. junction: $I_3 = I_1 + I_2$
2. left loop: $20 - 5I_1 + 10I_2 = 0$
3. right loop: $-2 - 10I_2 - 10I_3 = 0$

solution: substitute Eq.1 for I_3 in Eq. 3:
rearrange: $-10I_1 - 20I_2 = 2$
rearrange Eq. 2: $5I_1 - 10I_2 = 20$

Now we have 2 eq., 2 unknowns.