

**Example** Time Constant Demo

Each circuit has a 0.5 F capacitor charged to 9 Volts.  
When the switch is closed:

- Which system will be brightest?
- Which lights will stay on longest?
- Which lights consume more energy?

1

$\tau = 2RC$

2

$\tau = RC/2$

**Checkpoint**  
RC Circuits 1 & 3

Both switches are initially open, and the capacitor is uncharged.  
What is the current through the battery just after switch  $S_1$  is closed?

- 1)  $I_b = 0$
- 2)  $I_b = \epsilon / (3R)$
- 3)  $I_b = \epsilon / (2R)$
- 4)  $I_b = \epsilon / R$

Both switches are initially open, and the capacitor is uncharged.  
What is the current through the battery after switch 1 has been closed a long time?

- 1)  $I_b = 0$
- 2)  $I_b = V / (3R)$
- 3)  $I_b = V / (2R)$
- 4)  $I_b = V / R$

**Example** Practice

Calculate current immediately after switch is closed:

Calculate current after switch has been closed for 0.5 seconds:

Calculate current after switch has been closed for a long time:

Calculate charge on capacitor after switch has been closed for a long time:

$R = 10\Omega$   
 $C = 30 \text{ mF}$   
 $\epsilon = 20 \text{ Volts}$

Both switches are closed. What is the final charge on the capacitor after the switches have been closed a long time?

1.  $Q = 0$
2.  $Q = C \epsilon / 3$
3.  $Q = C \epsilon / 2$
4.  $Q = C \epsilon$

**Example** Charging: Intermediate Times

Calculate the charge on the capacitor  $3 \times 10^{-3}$  seconds after switch 1 is closed.

$q(t) = q_{\infty}(1 - e^{-t/RC})$

$R_1 = 20 \Omega$   
 $R_2 = 40 \Omega$   
 $\epsilon = 50 \text{ Volts}$   
 $C = 100 \mu\text{F}$


**RC Circuits: Discharging**

- KLR: \_\_\_\_\_
- Just after...: \_\_\_\_\_  
– Capacitor is still fully charged
- Long time after: \_\_\_\_\_
- Intermediate (more complex)  
–  $q(t) = q_0 e^{-t/RC}$   
–  $I_C(t) = I_0 e^{-t/RC}$

Checkpoint RC Circuits 5


- After switch 1 has been closed for a long time, it is opened and switch 2 is closed. What is the current through the right resistor just after switch 2 is closed?

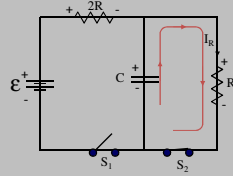- $I_R = 0$
- $I_R = \epsilon / (3R)$
- $I_R = \epsilon / (2R)$
- $I_R = \epsilon / R$



After being closed for a long time, the switch is opened. What is the charge  $Q$  on the capacitor 0.06 seconds after the switch is opened?

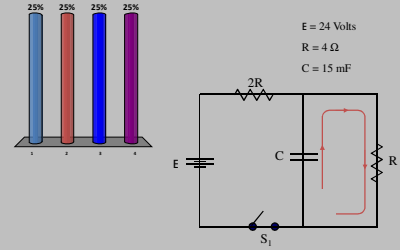- $0.368 q_0$
- $0.632 q_0$
- $0.135 q_0$
- $0.865 q_0$



$E = 24$  Volts  
 $R = 4 \Omega$   
 $C = 15$  mF