

Physics 1161: Lecture 14


Transformers

- **Textbook Sections 23-7 – 23-8**

Transformers

Key to efficient power distribution

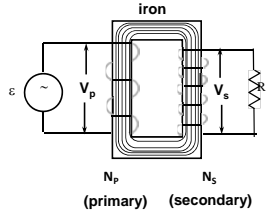
Increasing current in primary creates an increase in flux through primary and secondary.



Transformers

- Key to Modern electrical system
- Starting with 120 volts AC
 - Produce arbitrarily small voltages.
 - Produce arbitrarily large voltages.
- Nearly 100% efficient


Checkpoint
Transformer 1

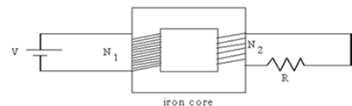

The voltage difference across the resistor R is

1. V
2. $V N_1/N_2$
3. $V N_2/N_1$
4. 0


Checkpoint
Transformer 2

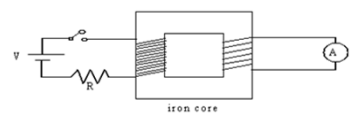

When the switch is closed, the ammeter shows

1. $I=0$
2. I quickly jumps to a non-zero value and then quickly returns to zero.
3. I is a steady non-zero value.

Checkpoint
Transformer 3

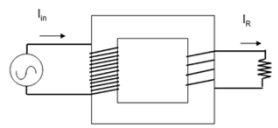

How does I_R compare to the current that is drawn from the AC source I_{in} ?


1. $I_R < I_{in}$
2. $I_R = I_{in}$
3. $I_R > I_{in}$

Checkpoint

Transformer


The good news is you are going on a trip to France. The bad news is that in France the outlets have 240 volts. You remember from Phy1152 that you need a transformer, so you wrap 100 turns around the primary. How many turns should you wrap around the secondary if you need 120 volts out to run your hair dryer?

- 1) 50 2) 100 3) 200

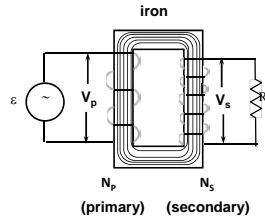

A 12 Volt battery is connected to a transformer that has a 100 turn primary coil, and 200 turn secondary coil. What is the voltage across the secondary after the battery has been connected for a long time?

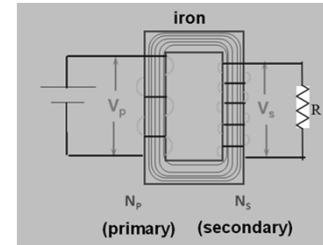1. $V_s = 0$
2. $V_s = 6 \text{ V}$
3. $V_s = 12 \text{ V}$
4. $V_s = 24 \text{ V}$



In a transformer the side with the most turns always has the larger peak voltage. (T/F)

1. True
2. False

In a transformer the side with the most turns always has the larger peak current. (T/F)

1. True
2. False

In a transformer the side with the most turns always dissipates the most power. (T/F)

1. True
2. False