




Electric Circuits




Count Alessandro Volta
(1745 - 1827)



Georg Simon Ohm
(1787 - 1854)




André Marie AMPÈRE
(1775 - 1836)



Charles Augustin de Coulomb
(1736 - 1806)

Simple Electric Cell

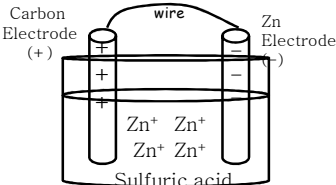

- Two dissimilar metals or carbon rods in acid
- Zn²⁺ ions enter acid leaving terminal negative
- Electrons leave carbon leaving it positive
- Terminals connected to external circuit
- 'Battery' referred to several cells originally

Electric Current


Electrons flow out of the negative terminal and toward the positive terminal → electric current. (We will consider conventional current - positive charges move)

Electric current I is defined as the rate at which charge flows past a given point per unit time.



$1 \text{ C/s} = 1 \text{ A}$ (ampere)

Electric Circuit

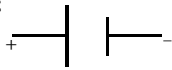- It is necessary to have a complete circuit in order for current to flow.
- The symbol for a battery in a circuit diagram is:



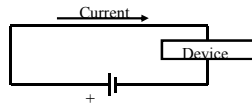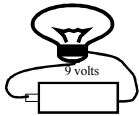"Conventional" current direction is opposite to actual electron flow direction which is - to +.



Ohm's Law

- For wires and other circuit devices, the current is proportional to the voltage applied to its ends:

$$I \propto V$$

- The current also depends on the amount of resistance that the wire offers to the electrons for a given voltage V .

- We define a quantity called *resistance* R such that

$$I = \frac{V}{R} \quad (\text{Ohm's Law})$$

- The unit of resistance is the ohm which is represented by the Greek capital omega (Ω).



$$1 \Omega = \frac{V}{A}$$

Resistors



- A resistor is a circuit device that has a fixed resistance.

[Resistor Code Calculator](#)

[Resistor Code](#)

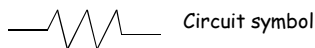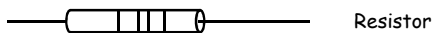


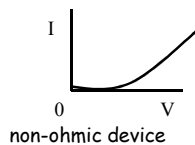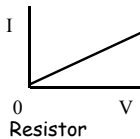Resistors obey Ohm's law but not all circuit devices do.




Ohm's Law

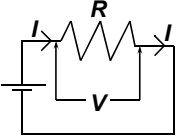- **Demo:**
 - Vary applied voltage V .
 - Measure current I
 - Does ratio $\frac{V}{I}$ remain constant?



$$R \equiv \frac{V}{I}$$

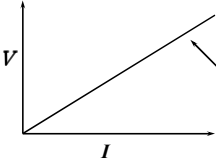


slope = R

How to calculate the resistance?
Include "resistivity" of material
Include geometry of resistor

Resistance

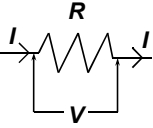
- **Resistance**
 Resistance is defined to be the ratio of the applied voltage to the current passing through.



$$R \equiv \frac{V}{I}$$

UNIT: OHM = Ω

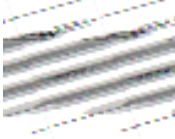- Increase the length \rightarrow flow of electrons impeded
- Increase the cross sectional area \rightarrow flow facilitated
- Compare to straws or pipes



Two cylindrical resistors are made from the same material, and they are equal in length. The first resistor has diameter d , and the second resistor has diameter $2d$.

- 1) Compare the resistance of the two cylinders.

a) $R_1 > R_2$
b) $R_1 = R_2$
c) $R_1 < R_2$
- 2) If the same current flows through both resistors, compare the average velocities of the electrons in the two resistors:

a) $v_1 > v_2$
b) $v_1 = v_2$
c) $v_1 < v_2$

Strain Gauge

- A very thin metal wire patterned as shown is bonded to some structure.
- As the structure is deformed slightly, this stretches the wire (slightly).
- When this happens, the resistance of the wire:



- (a) decreases (b) increases (c) stays the same

Because the wire is slightly longer, $R \sim L/A$ is slightly increased. Also, because the overall volume of the wire is ~constant, increasing the length decreases the area A , which also increases the resistance. By carefully measuring the change in resistance, the strain in the structure may be determined.

Power in Electric Circuits

- Electrical circuits can transmit and consume energy.
- When a charge Q moves through a potential difference V , the energy transferred is QV .
- Power is energy/time and thus:

$$P = \text{power} = \frac{\text{energy}}{\text{time}} = \frac{QV}{t} = \left(\frac{Q}{t}\right) V = IV$$

and thus:

$$P = IV$$

Notes on Power

- The formula for power applies to devices that provide power such as a battery as well as to devices that consume or dissipate power such as resistors, light bulbs and electric motors.

$$A \cdot V = \frac{C}{s} \cdot \frac{J}{C} = \frac{J}{s} = \text{Watt}(W)$$

- The formula for power can be combined with Ohm's Law to give other versions:

$$P = IV = I^2 R = \frac{V^2}{R}$$

Household Power

• Electric companies usually bill by the **kilowatt-hour (kWh.)** which is the energy consumed by using 1.0 kW for one hour.

• Thus a 100 W light bulb could burn for 10 hours and consume 1.0 kWh.


• Electric circuits in a building are protected by a fuse or circuit breaker which shuts down the electricity in the circuit if the current exceeds a certain value. This prevents the wires from heating up when carrying too much current.

Resistors in Series

The Voltage "drops":


$$V_a - V_b = IR_1 \quad V_b - V_c = IR_2$$

$$V_a - V_c = I(R_1 + R_2)$$

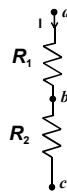


Whenever devices are in **SERIES**, the current is the same through both!

This reduces the circuit to:

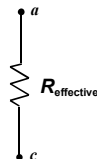

Hence: $R_{\text{effective}} = (R_1 + R_2)$

Voltage Divider

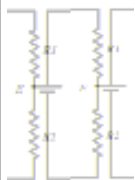

Two resistors are connected in series to a battery with emf E . The resistances are such that $R_1 = 2R_2$.

Compare the current through R_1 with the current through R_2 :


- a) $I_1 > I_2$
- b) $I_1 = I_2$**
- c) $I_1 < I_2$

What is the potential difference across R_2 ?

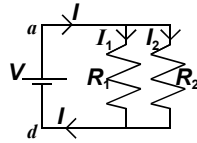- a) $V_2 = E$
- b) $V_2 = 1/2 E$
- c) $V_2 = 1/3 E$**

Resistors in Parallel

- What to do? $V = IR$
- Very generally, devices in parallel have the same voltage drop
- But current through R_1 is not I ! Call it I_1 . Similarly, $R_2 \leftrightarrow I_2$.




KVL \Rightarrow $V - I_1 R_1 = 0$
 $V - I_2 R_2 = 0$

- How is I related to I_1 & I_2 ?

Current is conserved!

$$I = I_1 + I_2$$
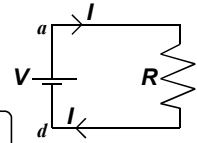
$$\Rightarrow \frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2} \Rightarrow \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$




Circuit Practice

- Consider the circuit shown:

1

– What is the relation between $V_a - V_d$ and $V_a - V_c$?

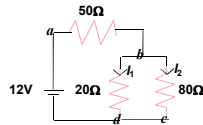- (a) $(V_a - V_d) < (V_a - V_c)$
 (b) $(V_a - V_d) = (V_a - V_c)$
 (c) $(V_a - V_d) > (V_a - V_c)$



2

– What is the relation between I_1 and I_2 ?

- (a) $I_1 < I_2$ (b) $I_1 = I_2$ (c) $I_1 > I_2$


Circuit Practice

- Consider the circuit shown:

1

– What is the relation between $V_a - V_d$ and $V_a - V_c$?

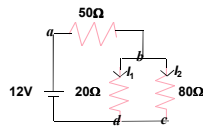- (a) $(V_a - V_d) < (V_a - V_c)$
 (b) $(V_a - V_d) = (V_a - V_c)$
 (c) $(V_a - V_d) > (V_a - V_c)$



• Point d and c are the same, electrically

Circuit Practice


• Consider the circuit shown:

– What is the relation between $V_a - V_d$ and $V_a - V_c$?

(a) $(V_a - V_d) < (V_a - V_c)$

(b) $(V_a - V_d) = (V_a - V_c)$

(c) $(V_a - V_d) > (V_a - V_c)$

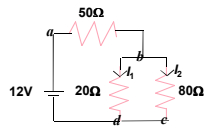

2 – What is the relation between I_1 and I_2 ?

(a) $I_1 < I_2$

(b) $I_1 = I_2$

(c) $I_1 > I_2$

• Note that: $V_b - V_d = V_b - V_c$

• Therefore,

$$I_1(20\Omega) = I_2(80\Omega) \Rightarrow I_1 = 4I_2$$

Summary of Simple Circuits


• Resistors in series: $R_{equivalent} = R_1 + R_2 + R_3 + \dots$

Current thru is same; Voltage drop across is IR_i

• Resistors in parallel: $\frac{1}{R_{equivalent}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$

Voltage drop across is same; Current thru is V/R_i

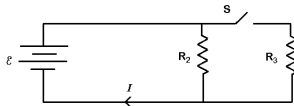Two identical light bulbs are represented by the resistors R_2 & R_3 ($R_2 = R_3$). The switch S is initially open.



If switch S is closed, what happens to the brightness of the bulb R_2 ?

a) It increases

b) It decreases

c) It doesn't change

What happens to the current I , after the switch is closed ?

a) $I_{after} = 1/2 I_{before}$

b) $I_{after} = I_{before}$

c) $I_{after} = 2 I_{before}$
